 


# Exercise 1: SystemVerilog

## 1. ALU

### a) DUT implementation

Implement the ALU as shown here:



```
package Types;
    typedef enum logic [1:0] {
        ADD      = 2'b00,
        SUBTRACT = 2'b01,
        MULTIPLY  = 2'b10
    } sel_t;

    typedef enum logic {
        WITH_CARRY = 1'b1,
        NO_CARRY   = 1'b0
    } mode_t;
endpackage : Types

module ALU(
    output logic [7:0] Result,
    output logic Equal,
    input logic [3:0] Op1,
    input logic [3:0] Op2,
    input sel_t Sel,
    input logic C_In,
    input mode_t Mode);
:
// your code goes here
:
endmodule : ALU
```

The inputs and outputs are defined as follows:

- Result: The result of the operation performed.
- Equal: High, if both operands are equal.
- C\_in: Carry-in
- Op1: The first operand.
- Op2: The second operand.
- Sel: The operation to perform.
  - ADD:  $Op1 + Op2$
  - SUBTRACT:  $Op1 - Op2$
  - MULTIPLY:  $Op1 \times Op2$

- others: *undefined*
- Mode: Enable or disable the carry input.

## b) Testing

- Write a testbench to verify that the ALU performs as expected.

## c) Clocking

- Add a Clock input to the ALU and place the result in a flip-flop.
- Adjust the testbench accordingly. Observe the delay between input and output changes.

*Hint:* Use @posedge (Clock); in your testbench code to wait for the next clock edge:

```
initial begin
    @posedge (Clock); // can go where #delay used to be
    // do something
end
```

## 2. SystemVerilog: Up-/Down-Counter

Implement a clocked counter that can count either up or down, and has

1. a sync. RESET
2. a sync. LOAD function (loading from DATA into the COUNT register).

Note: RESET shall take precedence over LOAD.

```
module UpDownCounter(
    input logic CLK,
    input logic RESET,
    input logic LOAD,
    input logic [5:0] DATA,
    input logic COUNT_UP, // == 1: count up, == 0: count down
    output logic [5:0] COUNT
);
:
// your code goes here
:
endmodule : UpDownCounter
```

## b) Testing

- Write a testbench exercising all modes of the counter.